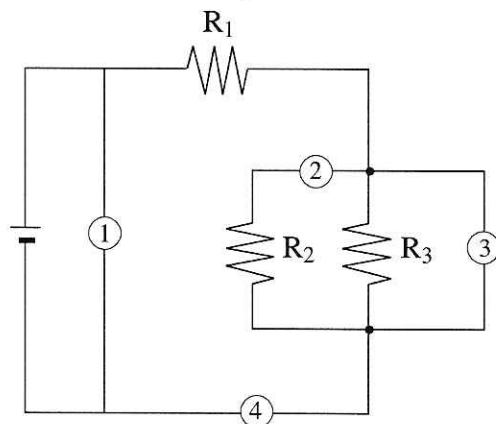



25. The diagram below shows a circuit with four possible meter locations.



In which locations should an ammeter and voltmeter be connected to correctly measure the current through  $R_2$  and the voltage drop across  $R_2$  ?


	CURRENT THROUGH $R_2$	VOLTAGE DROP ACROSS $R_2$
A.	2	1
B.	2	3
C.	4	1
D.	4	3

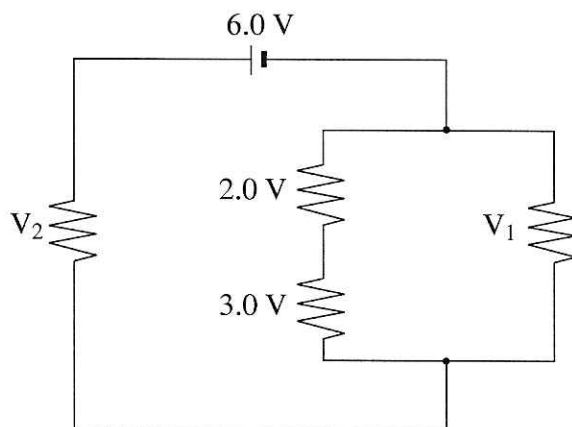26. What are the potential differences,  $V_1$  and  $V_2$ , in the circuit shown below?




	Potential Difference $V_1$	Potential Difference $V_2$
A.	1.0 V	5.0 V
B.	1.0 V	6.0 V
C.	5.0 V	1.0 V
D.	5.0 V	5.0 V

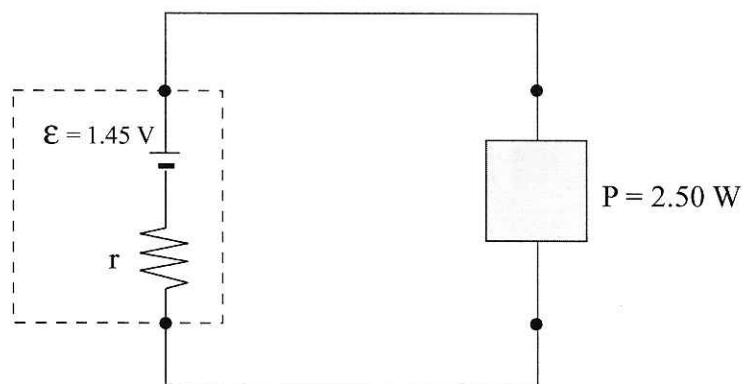27. A  $2.50\text{ W}$  device requires  $1.20\text{ V}$  to operate properly. A  $1.45\text{ V}$  cell, with internal resistance  $r$ , is used to power this device. What value of  $r$  enables the cell to provide  $1.20\text{ V}$  to the device?




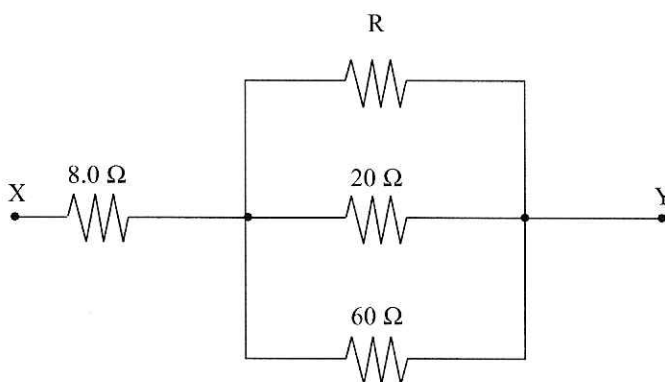- A.  $0.120\ \Omega$   
 B.  $0.145\ \Omega$   
 C.  $0.576\ \Omega$   
 D.  $0.841\ \Omega$
28. A  $660\text{ W}$  electric heater is designed to operate from a  $120\text{ V}$  source. If the source voltage drops to  $80.0\text{ V}$ , what will be the power dissipated by the same heater? (Assume the resistance of the heater is constant.)
- A.  $73.3\text{ W}$   
 B.  $293\text{ W}$   
 C.  $440\text{ W}$   
 D.  $660\text{ W}$
29. The total resistance between points X and Y is  $14.0\ \Omega$ . What is the value of R?



- A.  $6.0\ \Omega$   
 B.  $8.3\ \Omega$   
 C.  $10\ \Omega$   
 D.  $210\ \Omega$




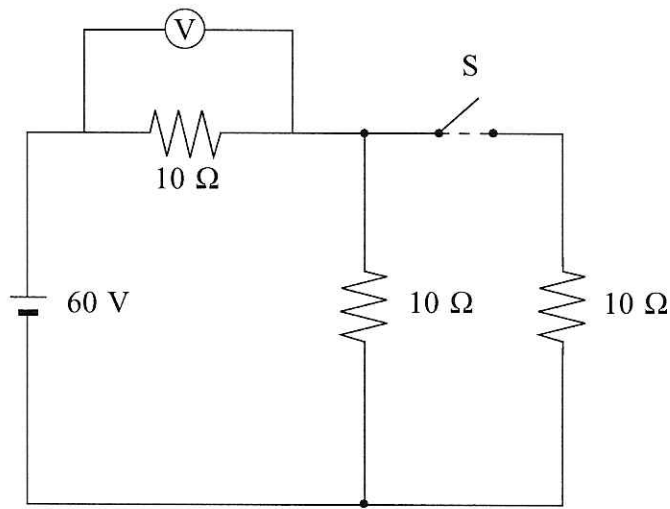
30. In the circuit shown below, voltmeter readings are taken when switch S is closed and open.




Which of the following is correct?

VOLTMETER READINGS	
SWITCH CLOSED	SWITCH OPEN
A. 20 V	30 V
B. 30 V	30 V
C. 40 V	20 V
D. 40 V	30 V

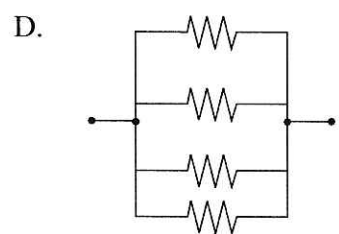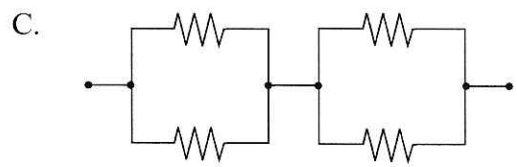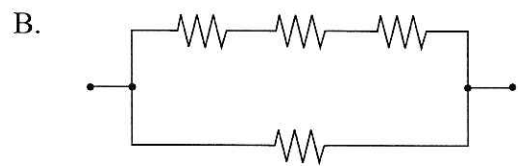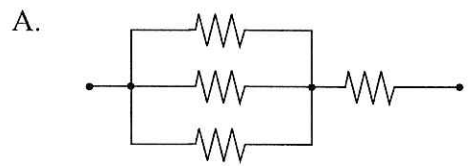31. Which of the following arrangements would draw the smallest current when connected to a potential difference? All resistors have the same value.




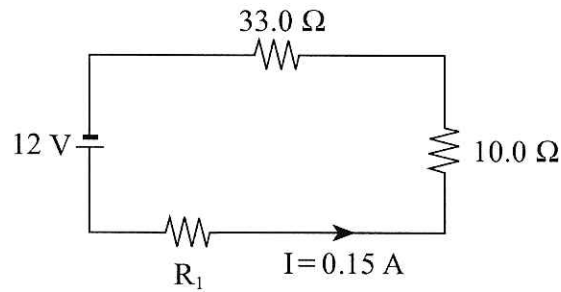32. What is the power dissipated in resistor  $R_1$  in the circuit shown in the diagram below?



- A. 0.83 W
- B. 0.97 W
- C. 1.8 W
- D. 2.8 W

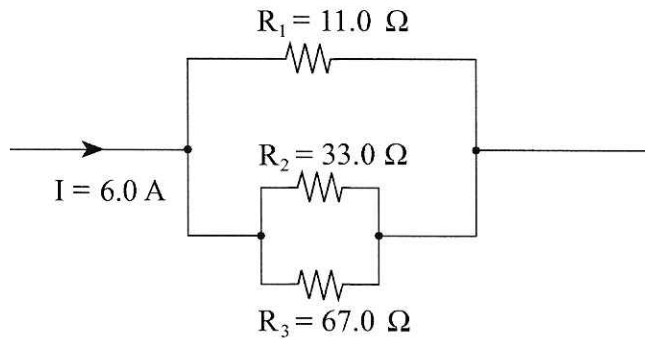
33. The diagram below shows part of an electrical circuit.



What is the current through resistor  $R_1$ ?


- A. 2.0 A
  - B. 3.0 A
  - C. 4.0 A
  - D. 6.0 A
34. A 75 W bulb is connected across a 120 V source. While the bulb is lighted, what is the effective resistance of the bulb?
- A. 0.62  $\Omega$
  - B. 1.6  $\Omega$
  - C. 47  $\Omega$
  - D. 190  $\Omega$

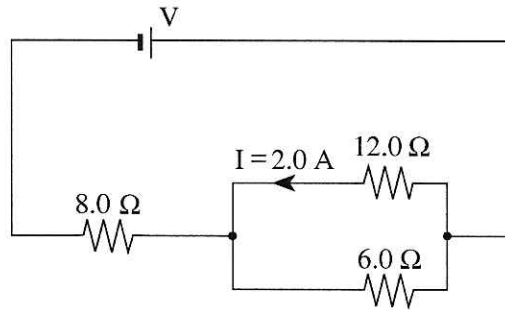35. What is the voltage,  $V$ , of the power supply shown in the circuit?





- A. 24 V
- B. 52 V
- C. 72 V
- D. 96 V

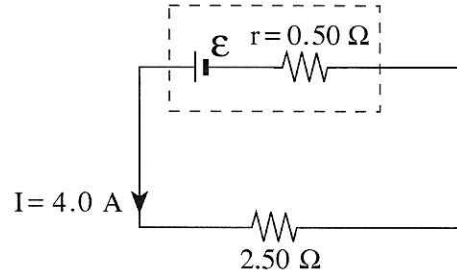36. What is the emf of the battery shown?




- A. 2.0 V
- B. 8.0 V
- C. 10 V
- D. 12 V

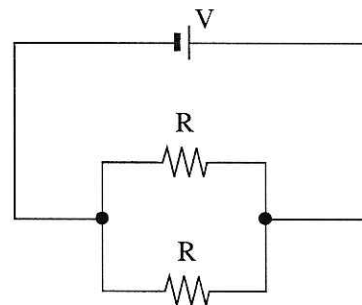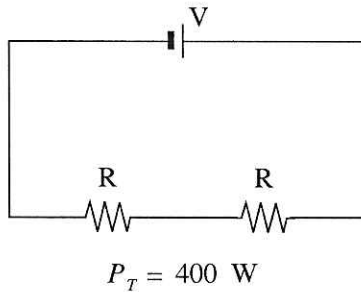37. Two identical resistors connected in series have a **total** power output of 400 W. Assuming  $V$  and  $R$  remain constant, what would the total power output be when the resistors are re-connected in parallel?




- A. 200 W
- B. 400 W
- C. 800 W
- D. 1600 W

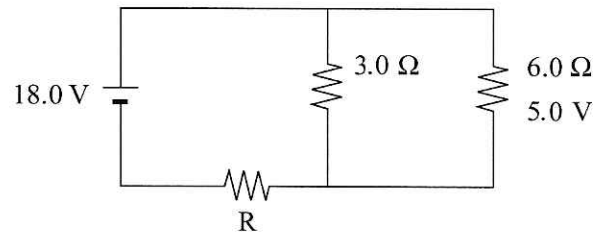38. In the following circuit, determine the value of resistor R.




- A.  $3.2 \Omega$
- B.  $5.2 \Omega$
- C.  $9.0 \Omega$
- D.  $23 \Omega$

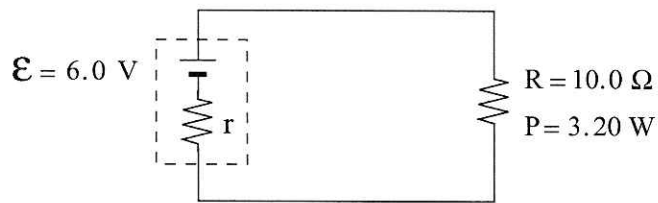39. A battery provides  $3.20 \text{ W}$  of power to an external resistance. What power is dissipated as heat by the internal resistance within the battery?



- A.  $0.19 \text{ W}$
- B.  $3.4 \text{ W}$
- C.  $3.6 \text{ W}$
- D.  $60 \text{ W}$

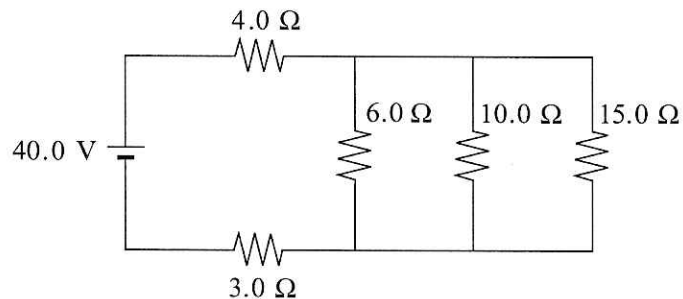
40. Calculate the current through the  $6.0 \Omega$  resistor in the circuit shown.



- A.  $1.1 \text{ A}$
- B.  $2.0 \text{ A}$
- C.  $4.0 \text{ A}$
- D.  $6.7 \text{ A}$

1. a) Find the current in the  $8.0 \Omega$  bulb shown below.

(5 marks)

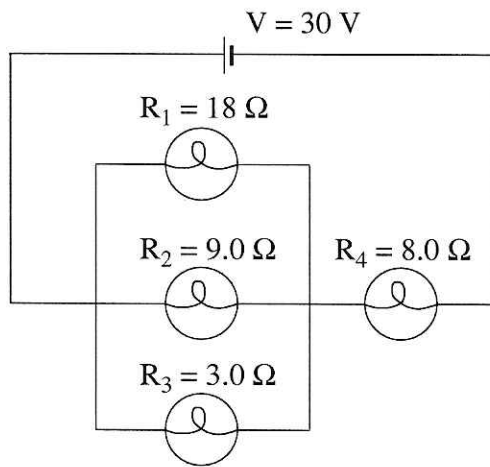

b) (i) The  $3.0\ \Omega$  bulb is removed from the circuit so that only 3 bulbs remain. The  $8.0\ \Omega$  bulb will now: **(Circle one)** **(1 mark)**

- A. be dimmer.
- B. be brighter.
- C. remain the same.

(ii) Using principles of electrical circuits, explain your answer to b(i). **(4 marks)**

---

---

---

---


---

---

---



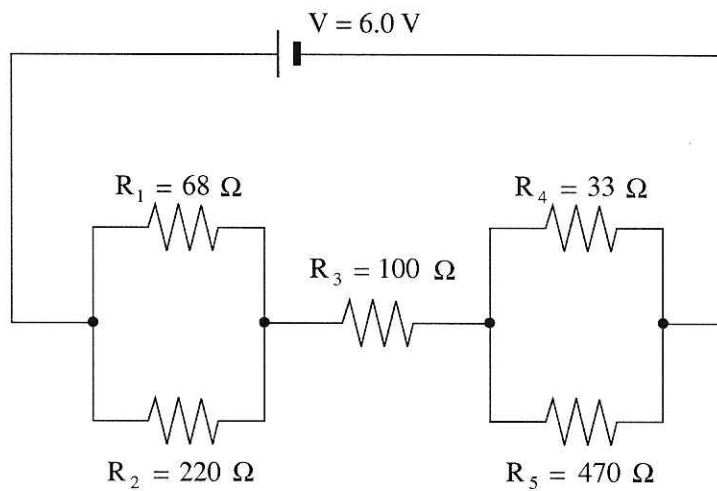2. Consider the circuit shown in the diagram below.



a) What is the total resistance of the circuit?

**(3 marks)**

b) What is the current through the  $100\ \Omega$  resistor?

**(2 marks)**

c) What is the power dissipated in the  $100\ \Omega$  resistor?

**(2 marks)**